





## Introduction to Bipolar Digital Circuits

### Analysis of BJT circuits with known states

BJT has four modes of operation

- ① cutoff mode
- ② forward active mode
- ③ saturation mode
- ④ reverse active mode

    \* The relationships for these modes are shown in the next figures:



\* Usually  $50 \leq \beta_F \leq 200$ .

#### Example 4.1 BJT Saturation


Determine the base and collector currents and  $\sigma$  for the saturated BJT in Figure 4.3. Let  $\beta_F = 65$ .

Since the BJT is in saturation mode & the emitter is at ground

$$V_B = V_{BE}(\text{sat}) = 0.8 \text{ V}$$

$$V_C = V_{CE}(\text{sat}) = 0.2 \text{ V}$$
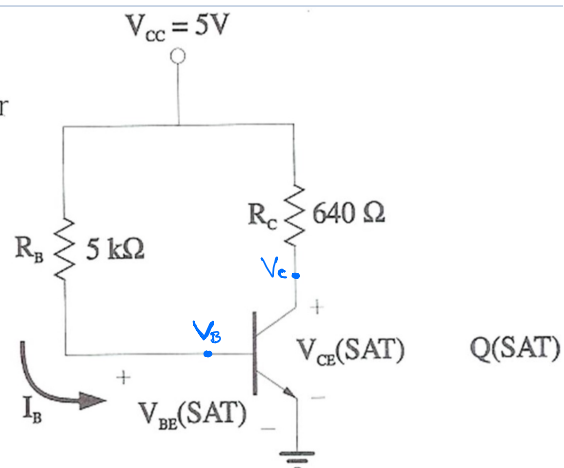
$$I_B = \frac{V_{CC} - V_{BE}(\text{sat})}{R_B} = \frac{5 - 0.8}{5\text{k}} = 840 \mu\text{A}$$




$$I_c = \frac{V_{cc} - V_{ce(sat)}}{R_c} = \frac{5 - 0.2}{640} = 7.5 \text{ mA}$$

$$I_{c(sat)} = \beta_f I_B \Rightarrow \beta = \frac{I_c}{\beta_f I_B} = \frac{7.5 \text{ m}}{65 \times 840 \mu} = 0.137$$

#### Example 4.2 BJT Analysis with Known States

Figure 4.4 shows a portion of a digital circuit where the state of each transistor is known. Solve for the voltages at the base and emitter of each BJT.

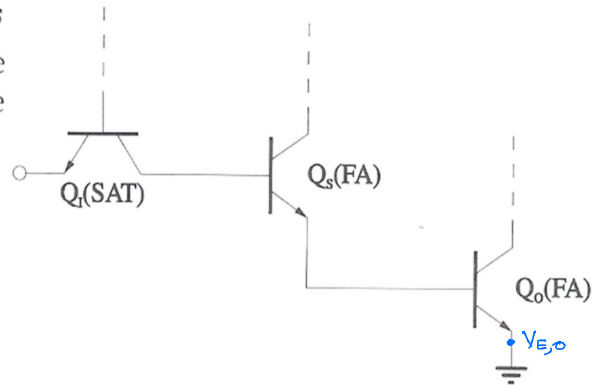

$Q_0$  is FA

$$V_{E,0} = 0 \text{ V}$$

$$V_{B,0} = V_{BE,0}(\text{FA}) = 0.7 \text{ V}$$

$Q_5$  is FA

$$V_{E,5} = V_{B,0} = 0.7 \text{ V}$$

$$V_{B,5} = V_{BE,0}(\text{FA}) + V_{BE,5}(\text{FA})$$

$$= 2V_{BE}(\text{FA}) = 2(0.7) = 1.4 \text{ V}$$

$Q_1$  is saturated

$$V_{E,1} = V_{BE,0}(\text{FA}) + V_{BE,5} - V_{CE,1}(\text{sat})$$

$$= 2(0.7) - 0.2 = 1.2 \text{ V}$$

$$V_{B,1} = V_{E,1} + V_{BE,1}(\text{sat})$$

$$= 1.2 + 0.8 = 2 \text{ V}$$

#### Example 4.3 Diode Analysis with Known States


Determine the current  $I$  through the branch in Figure 4.5. Also, find the voltage at the base of the transistor  $Q$ . Assume the BJT base current is negligible.

Using KVL

$$\text{GND} - IR_1 - IR_2 - V_{D1}(\text{on}) - V_{D2}(\text{on}) - IR_3 + V_{EE} = 0$$

$$I = \frac{V_{EE} - 2V_{D1}(\text{on})}{R_1 + R_2 + R_3} = \frac{5.2 - 2(0.7)}{(200) + (750) + (300)} = 3.04 \text{ mA}$$
 
$$V_B = \text{GND} - IR_1 = 0 - (3.04 \text{ m})(200) = -608 \text{ mV}$$



## Notes:

For diode

$$V_D(ON) = 0.7V$$

For BJT

$$FA: V_{BE} = 0.7V \text{ \& } I_C = \beta_F I_B$$

$$Sat: V_{BE} = 0.8V \text{ \& } V_{BC} = 0.6V \text{ \& } V_{CE} = 0.2V \text{ \& }$$

$$\alpha = \frac{I_C}{\beta_F I_B}$$

$$RA: V_{BC} = 0.7V \quad I_E = \alpha_R I_C = -\beta_R I_C$$

$$\beta_R = \frac{\alpha_R}{1 - \alpha_R}, \quad \beta_R \ll \beta_F \text{ \& } \beta_F = \frac{\alpha_F}{1 - \alpha_F}$$

For Schottky diode:

$$V_{SBD}(ON) = 0.3V$$

For Schottky clamped BJT:

$$F.A \text{ (SBD not conducting)}: V_{BE}(ON) = 0.7V$$

$$ON HARD: V_{BE}(HARD) = 0.8V$$

$$\text{ \& } V_{BC}(ON) = V_{SBD}(ON) = 0.3V$$

$$\text{ \& } V_{CE}(HARD) = 0.5V$$

\* Schottky-clamped BJT is simply a BJT with schottky barrier diode connected between the base & collector. This diode prevents the BJT from operating in the saturation region.

## BJT Inverter


\* The circuit consists of a BJT with base & collector resistors & one voltage source  $V_{CC}$ .

\* Output High Voltage  $\equiv V_{OH}$

$$\therefore V_{BE} < V_{BE}(FA)$$

$\therefore$  BJT is cutoff

$$\text{ \& } I_C = I_{RC} = 0$$

 

$\Rightarrow$  There is no voltage drop across  $R_C$

$$V_{out} = V_{CC} = V_{OH} \Rightarrow I_{C(OH)} = 0$$

\* Input Low Voltage  $\equiv V_{IL}$

when  $V_{BE} = V_{BE(FA)}$  the BJT is at the edge of conduction where the cutoff & forward active regions meet.

$$V_{IL} = V_{BE(FA)}$$

when  $V_{in}$  passes  $V_{BE(FA)}$  the voltage  $V_{in} - V_{BE(FA)}$  across  $R_B$  corresponds to  $I_B = I_{BF}$   
 $I_C = \beta_F I_B$  &  $V_{out}$  decreases by  $I_C R_C$

\* Output Low Voltage  $\equiv V_{OL}$

Increasing  $V_{in}$  to point of saturation

$$V_{OL} = V_{CE(sat)}$$

$V_{CE}$  is the minimum collector-emitter voltage.

\* Input High Voltage  $\equiv V_{IH}$

$V_{IH}$  is the input voltage at the edge of saturation & is also defined to be at the edge of the active region.

$$@ V_{CE} = V_{CE(sat)}$$

$$I_C = \frac{V_{CC} - V_{CE(sat)}}{R_C}$$


@ edge of saturation  $\sigma = 1 \Rightarrow I_C = \beta_F I_B$

$$I_{B(EOS)} = \frac{I_C}{\beta_F} = \frac{V_{CC} - V_{CE(sat)}}{\beta_F R_C}$$

$$\therefore V_{BE} = V_{BE(sat)}$$

$$V_{IH} = V_{BE(sat)} + I_{B(EOS)} R_B$$
 
$$= V_{BE(sat)} + \left( \frac{V_{CC} - V_{CE(sat)}}{\beta_F R_C} \right) R_B$$





### Example 4.4 BJT Inverter Voltage Transfer Characteristic

For the BJT inverter of Figure 4.6, determine the high and low noise margins for  $V_{CC} = 5\text{ V}$ ,  $R_B = 10\text{ k}\Omega$ ,  $R_C = 1\text{ k}\Omega$ , and  $\beta_F = 60$ .

$$V_{CC} = 5\text{ V} \quad R_B = 10\text{ k}\Omega \quad R_C = 1\text{ k}\Omega$$

$$\beta_F = 60$$

$$V_{OH} = V_{CC} = 5\text{ V}$$

$$V_{IL} = V_{BE(FA)} = 0.7\text{ V}$$

$$V_{OL} = V_{CE(sat)} = 0.2\text{ V}$$


$$V_{IH} = V_{BE(sat)} + \left( \frac{V_{CC} - V_{CE(sat)}}{\beta_F R_C} \right) R_B$$

$$= 0.8 + \frac{(5 - 0.2)}{60 \times 1\text{ k}} \times 10\text{ k} = 1.6\text{ V}$$

$$V_{NMH} = V_{OH} - V_{IH} = 5 - 1.6 = 3.4\text{ V}$$

$$V_{NML} = V_{IL} - V_{OL} = 0.7 - 0.2 = 0.5\text{ V}$$

 \* The low noise margin of the simple BJT inverter is unacceptably small.



### TTL Super-Circuitry.

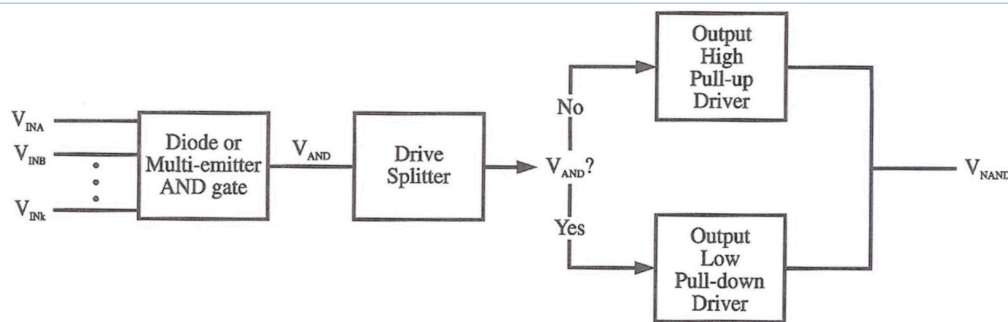


FIGURE 4.7 TTL Family Super-circuitry Block Diagram

### Input Section:

the input section consists of an ANDing of all inputs

## Drive Splitter

- \* the drive splitter turns on one of the two output sections
- \* A typical drive splitter is the BJT inverter we saw previously
- \* If the output of the AND gate is logic low the input voltage to the drive splitter is also low.
- \* For a logic high output from the AND gate the opposite output results
- \* the two output drivers are never on simultaneously,
- \* the drive splitter also provides additional base driving current to the output-low pull-down driver.
- \* while the input stage ANDs the multiple inputs the drive splitter section provides inversion
- \* if all inputs are connected together the logic circuit then reduces to an inverter

## Output-High Pull-Up Driver

- \* As the output goes low-to-high current is required to charge the equivalent capacitance of the load gates & the output-high pull-up section provides sourcing current for this charging

- \* It can be represented as

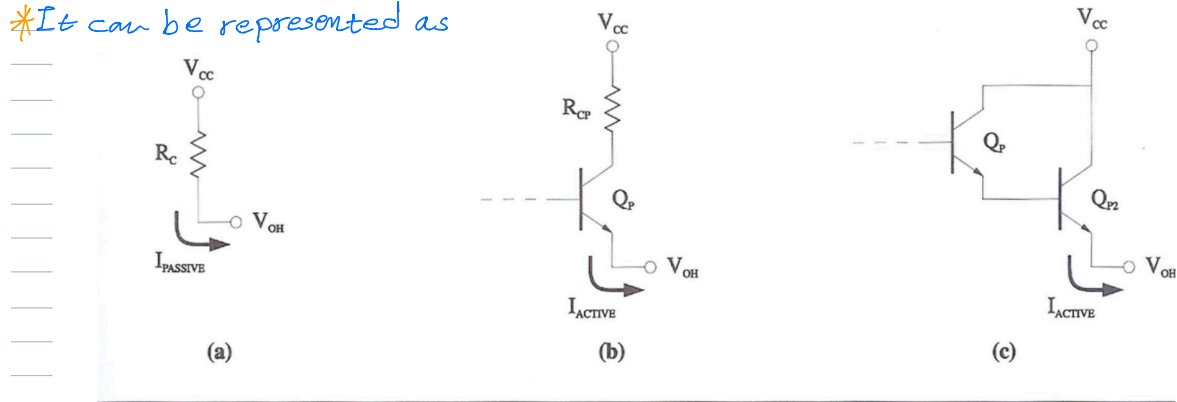


FIGURE 4.8 Pull-up Current Sources: (a) Passive, (b) Active, (c) Darlington pair active

- (a) voltage driven resistor
- (b) An emitter-follower which provides a higher sourcing current & therefore, faster switching time.
- (c) Darlington pair configuration provides the highest sourcing current among these three & it provides greater fan-out

## Output-Low Pull-Down Driver

- \* Provides large sinking current to discharge the capacitive load
- \* Provides larger fan-out by sinking (non-zero) currents  $I_{Li}$  from all the load gates
- \* The current  $I_{OL}$  is collector current for a BJT and allows enough fan-out.

 


FIGURE 4.9 Fan-out Current Sinking


## Level Shifting BJTs

The conducting diode voltage  $V_{D(ON)} = 0.7V$  is an ideal element for level-shifting but alternatively the BE portion of a BJT can also be used for level-shifting and has the advantage of providing additional driving current.
 
### Example 4.5 Level-Shifting

What is the level-shifting voltage  $V_{SHIFT}$  of the BJT-diode pair in Figure 4.10? Assume the BJT is forward-active and the diode is conducting.


$$\begin{aligned} V_{SHIFT} &= V_{BE(FA)} + V_{D(ON)} \\ &= 0.7 + 0.7 = 1.4V \end{aligned}$$




## Discharge Paths & Base Driving Circuitry

- \* In order to turn off a saturated BJT, all of the stored charge in the base region must be removed. A path must therefore be available for base discharge.
- \* The resistor  $R_D$  provides passive charge removal
- \* The current magnitude is the base voltage of  $Q_0$  divided by the resistor

$$I_{RD} = \frac{V_{B0}}{R_D}$$

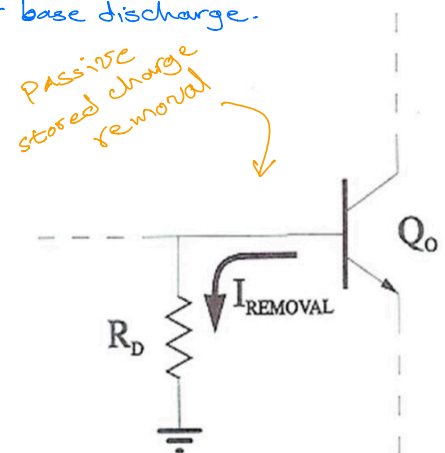


 - \* Active configuration for stored charge removal provides a much faster discharge than  $R_D$ .



Active stored charge removal

 - \* The turn on time of a BJT is dependent on the time required to charge the base of the BJT.
- \* Active base driving current is often supplied to BJTs that require a brief switching time.
- \* Emitter follower BJT configuration usually provides this driving current.
- \* The figure to the right shows an emitter-follower  $Q_S$  that provides base driving current to  $Q_O$ .



## Self-Biasing BJTs

- \* If the resistors  $R_B$  &  $R_C$  of the self-biasing BJT are chosen properly the BJT will operate in the FA region.

$$V_{BE(FA)} = 0.7V \quad \& \quad I_C = \beta_F I_B$$


- \* The usual application of the self-biasing BJT is as current sink

- \* The desired value of  $V_{CE}$  must be selected before values for the resistors can be chosen.

$$I_B = \frac{V_{CC} - V_{BE(FA)}}{R_B}$$

$$I_C = \beta_F I_B = \frac{V_{CC} - V_{CE}}{R_C}$$
 
$$\frac{R_B}{R_C} = \beta_F \frac{V_{CC} - V_{BE(FA)}}{V_{CC} - V_{CE}}$$



Self-Biasing BJT

$$\frac{R_B}{R_C} \approx \beta_F \quad \text{because} \quad V_{BE} \approx V_{CE}$$


\*  $R_B$  should be the largest resistance since  $I_B < I_C$

\* The ratio  $R_B/R_C$  determines how hard the BJT is driven & thus the magnitude of stored charge in the base

 
#### Example 4.6 Self-Biasing BJT

Determine the ratio  $R_B/R_C$  for a self-biasing BJT with  $V_{CE} = 0.6 \text{ V}$ . Let  $V_{CC} = 4 \text{ V}$  and  $\beta_F = 60$ .

$$\begin{aligned} \frac{R_B}{R_C} &= \beta_F \frac{V_{CC} - V_{BE(FA)}}{V_{CC} - V_{CE}} \\ &= 60 \times \frac{4 - 0.7}{4 - 0.6} = 58.2 \end{aligned}$$



 
\* The self-biasing BJT is exploited in BJT digital circuits for the purposes of sinking current sources and driving currents



Current sinking self-biasing BJT

configuration in which an incoming current is said to be sunk

 configuration where the operating voltage is determined by a node voltage of another portion of the circuit.



Self-biasing BJT operating from neighboring node voltage

## Power Dissipation of Bipolar Logic Circuits

\*For bipolar logic circuits that have a single power supply:

$$P_{cc} = I_{cc} V_{cc}$$

$I_{cc} \equiv$  the current supplied by  $V_{cc}$  and it is obtained by summing all the currents leaving the supply voltage source.

For the bipolar logic gate of the figure to the right the current supplied by  $V_{cc}$  is

$$I_{cc} = I_{RB} + I_{RC} + I_{RCP}$$

The average power dissipated in a logic circuit with two output is defined as:

$$P_{cc(avg)} = \left( \frac{I_{cc(OH)} + I_{cc(OL)}}{2} \right) V_{cc}$$

### Example 4.7 Average Power Dissipation

Figure 4.15 shows the top portion of a bipolar logic gate. The resistor currents for the output high state are  $I_{RB}(OH) = 1.55 \text{ mA}$ ,  $I_{RC}(OH) = 24.7 \text{ } \mu\text{A}$ ,  $I_{RCP}(OH) = 1.21 \text{ mA}$ , and for the output low state  $I_{RB}(OL) = 1.14 \text{ mA}$ ,  $I_{RC}(OL) = 4.48 \text{ mA}$ , and  $I_{RCP}(OL) = 104 \text{ } \mu\text{A}$ . What is the average power dissipated in this gate?

$$\begin{aligned} I_{cc(OH)} &= I_{RB(OH)} + I_{RC(OH)} + I_{RCP(OH)} \\ &= 1.55 \text{ m} + 24.7 \text{ } \mu\text{A} + 1.21 \text{ m} \\ &= 2.78 \text{ mA} \end{aligned}$$

$$\begin{aligned} I_{cc(OL)} &= I_{RB(OL)} + I_{RC(OL)} + I_{RCP(OL)} \\ &= 1.14 \text{ m} + 4.48 \text{ m} + 104 \text{ } \mu\text{A} \\ &= 5.72 \text{ mA} \end{aligned}$$

$$P_{cc(avg)} = \left( \frac{I_{cc(OH)} + I_{cc(OL)}}{2} \right) V_{cc} = \left( \frac{2.78 \text{ m} + 5.72 \text{ m}}{2} \right) \times 5$$

$$P_{cc(avg)} = 21.3 \text{ mW}$$

 


FIGURE 4.13 Power Supplied to a Logic Gate

 


FIGURE 4.14 Current Supplied to a Bipolar Logic Gate

